

The RC Time Constant

Lab #3

Name: Avery Karlin
Partner: Jeffrey Zou

The RC Time Constant

Objective

The objective of the lab is to measure the time constant of an RC circuit based on the rate of charging and discharging.


Introduction

Capacitors are defined by the equation $Q = CV$, such that the voltage of the capacitor is directly proportional to the charge, with the proportionality constant called the capacitance. Similar, resistor voltage is defined by Ohm's Law, such that $V = IR$. Thus, for a circuit purely with a resistor and a capacitor (RC circuit), the differential equation by Kirchoff's Voltage Law states that for charging (connected to the battery), $V_0 = \frac{Q}{C} + R\frac{dQ}{dt}$, and when discharging (disconnected from the battery), $0 = \frac{Q}{C} + R\frac{dQ}{dt}$. Thus, this can be solved to get an equation for charging, $V = V_0(1 - e^{-\frac{t}{RC}}) = V_0(1 - e^{-\frac{t}{\tau}})$ and for discharging, $V = V_0e^{-\frac{t}{RC}} = V_0e^{-\frac{t}{\tau}}$, where $\tau = RC$, called the time constant for an RC circuit.

These equations can be modified such that for charging, $-\ln(\frac{V_0-V}{V_0}) = -\frac{t}{RC}$ and for discharging, $-\ln(\frac{V}{V_0}) = -\frac{t}{RC}$. Since the left-hand side here forms a constant term and the right is a constant multiplied by t, it forms a line with the slope equal to $\frac{-1}{RC}$.

Procedures and Results

First, the power source is connected to a capacitor and then a variable resistor set to some value, joined back to the power source, with a voltmeter connected to the capacitor to measure the capacitor's charging voltage. After the power source is activated, it is timed with a stopwatch as it charges, recording the voltage as time increases, until the voltage of the capacitor is negligibly less than the battery, and it can't increase further. After, it is disconnected from the power source, such that the resistor is directly connected to the capacitor, such that it acts as the power source, discharging as voltage is lost through the resistor, recording the voltage as time increases again until it has only a negligible amount of voltage remaining. This is then repeated for a capacitor of a different capacitance.

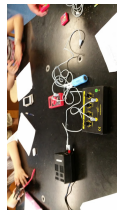

Capacitor 1:

$$C = 5100\mu F$$



$$R = 1350\Omega$$

Charging Time (s)	Charging Voltage (V)	Discharging Voltage (V)
0	0	8.87
4	3.48	5.48
8	5.47	3.37
12	6.8	2.12
16	7.53	1.43
20	8.06	0.9
24	8.31	0.6
28	8.51	0.38
32	8.63	0.26
36	8.72	0.17
40	8.77	0.12

Capacitor 2:

$$C = 4200\mu F$$

$$R = 1350\Omega$$

Charging Time (s)	Charging Voltage (V)	Discharging Voltage (V)
0	0	8.91
4	5.18	4.74
8	7.16	2.30
12	7.84	1.13
16	8.26	0.6
20	8.60	0.33
24	8.75	0.16
28	8.81	0.10
32	8.87	0.06
36	8.89	0.03
40	8.90	0.02

Discussion

Sample calculations for the non-measured data are as shown using the formulas found above:

$$R(\text{Voltmeter Interference, Small Resistor, Trial 1}) = \frac{V}{I - \frac{V}{R_V}} = \frac{2.6}{0.048 - \frac{2.6}{10^7}} = 54.16\Omega$$

$$R(\text{Ammeter Interference, Small Resistor, Trial 1}) = \frac{V}{I} - R_A = \frac{2.6}{0.048} - 0.48 = 53.69\Omega$$

$$R_{avg}(\text{Voltmeter Interference, Small Resistor}) = \frac{R_1 + R_2 + R_3}{3} = \frac{54.16 + 53.85 + 51.61}{3} = 53.21\Omega$$

$$\text{Percent Error (Small Resistor, Voltmeter Interference)} = \frac{|\text{Expected} - \text{Actual}| * 100\%}{\text{Expected}} =$$

$$\frac{|50.2 - 53.21| * 100\%}{53.21} = 5.66\%$$

$$R(\text{Wheatstone, Small Resistor, Trial 1}) = \frac{R_2 R_K}{R_1} = \frac{12.8 * 50.2}{24.2} = 26.55\Omega$$

Small Resistor:

Rheostat Setting	1	2	3
Resistance, R (Ω)	54.16	53.85	51.61

Average Resistance (Ω) = 53.21

Percent Error = 5.66%

Rheostat Setting	1	2	3
Resistance, R (Ω)	53.69	53.37	49.52

Average Resistance (Ω) = 52.19

Percent Error = 3.96%

Large Resistor:

Rheostat Setting	1	2	3
Resistance, R (Ω)	78.79	79.31	79.17

Average Resistance (Ω) = 79.09

Percent Error = 5.88%

Rheostat Setting	1	2	3
Resistance, R (Ω)	80.77	78.83	80.47

Average Resistance (Ω) = 80.02

Percent Error = 7.12%

Wheatstone Bridge:

Trial	1	2	3
Resistance, R (Ω)	26.55	26.87	25.6

Average Resistance (Ω) = 26.34

Percent Error = 2.9%

Trial	1	2	3
Resistance, R (Ω)	76.8	76.56	78.55

Average Resistance (Ω) = 77.3

Percent Error = 3.48%

The most likely cause of error is compounding loss of specificity due to the incorrect settings used on the multimeters. In addition, since the large resistors tend to have greater percent error than the other resistors, it indicates the measurement for that resistor's resistance may have been too low in some regard. Otherwise though, the overall percent error for each of the pieces of data was relatively low, such that it is mainly accurately done.

Conclusion

The measured average resistance of the small resistor with the voltmeter needing to be accounted for, with an actual resistance of 50.2Ω , was 53.21Ω with a percent error of 5.66%. The measured average resistance of the small resistor with the ammeter needing to be accounted for, with an actual resistance of 50.2Ω , was 52.19Ω with a percent error of 3.96%. The measured average resistance of the large resistor with the voltmeter needing to be accounted for, with an actual resistance of 74.7Ω , was 79.09Ω with a percent error of 5.88%. The measured average resistance of the large resistor with the ammeter needing to be accounted for, with an actual resistance of 74.7Ω , was 80.02Ω with a percent error of 7.12%. The measured average resistance of the small resistor by the wheatstone bridge, with an actual resistance of 25.6Ω , was 26.34Ω with a percent error of 2.9%. The measured average resistance of the large resistor by the wheatstone bridge, with an actual resistance of 74.7Ω , was 77.3Ω with a percent error of 3.48%.